
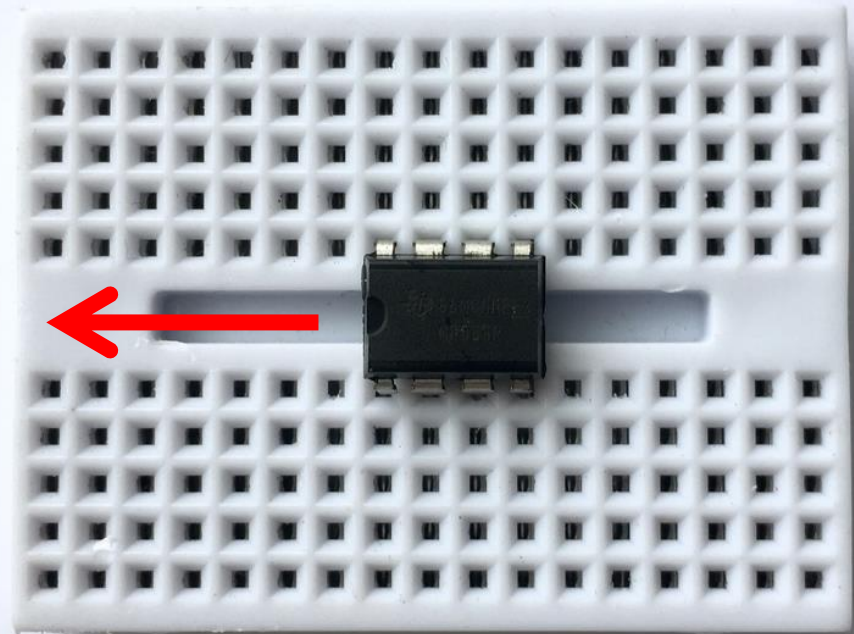




step1

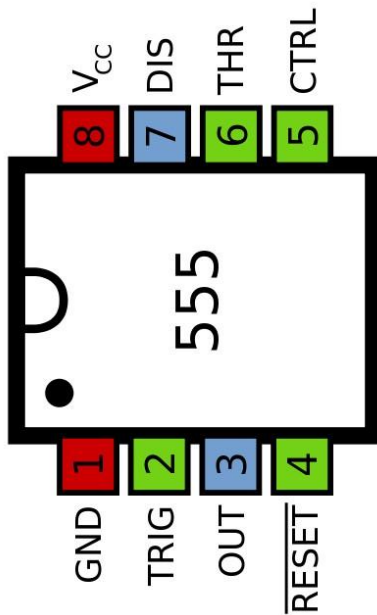
put the 555 IC on a breadboard and pin 1 to
the left side



step2


use jumper wire connector pin4 and pin8

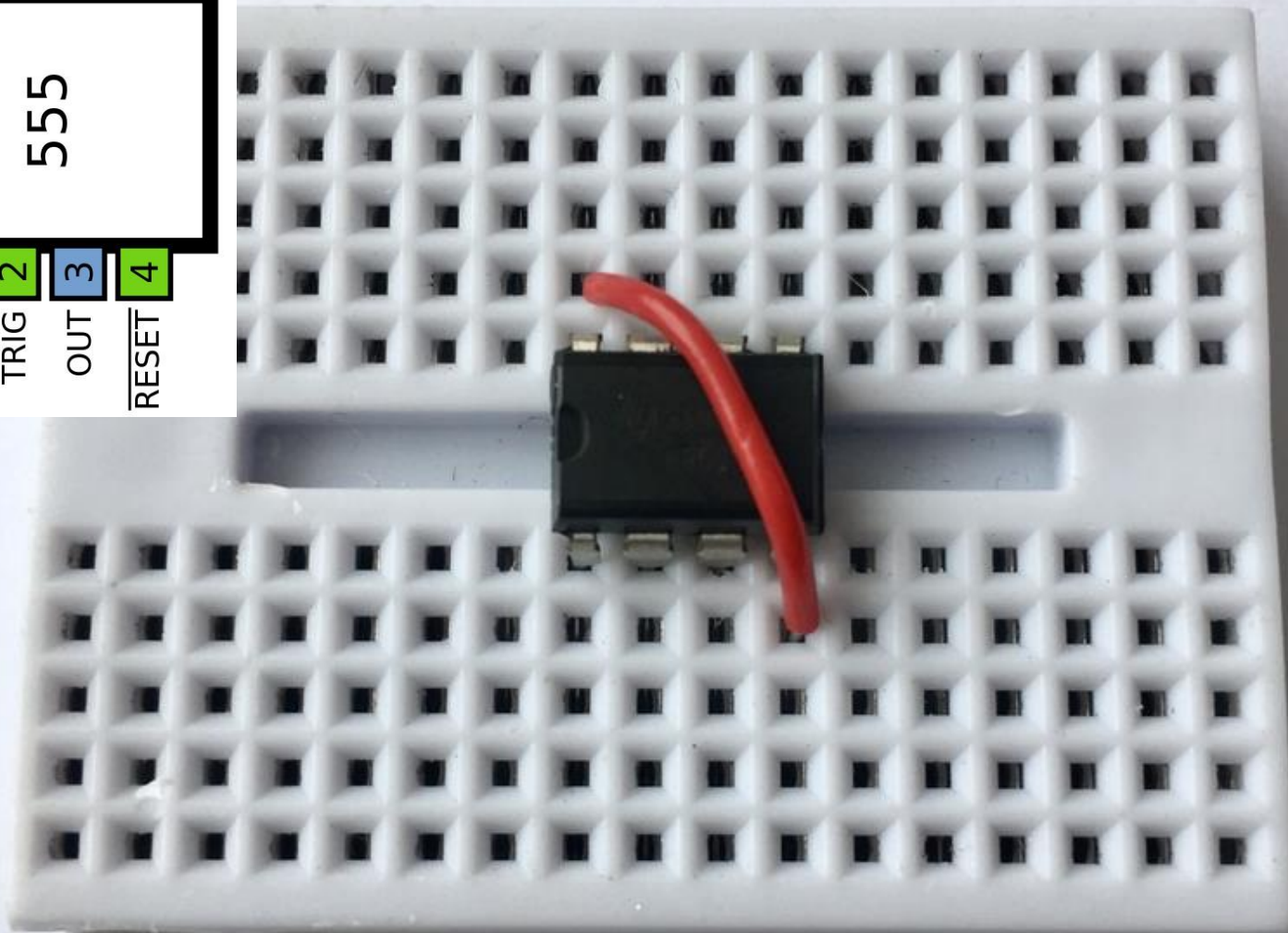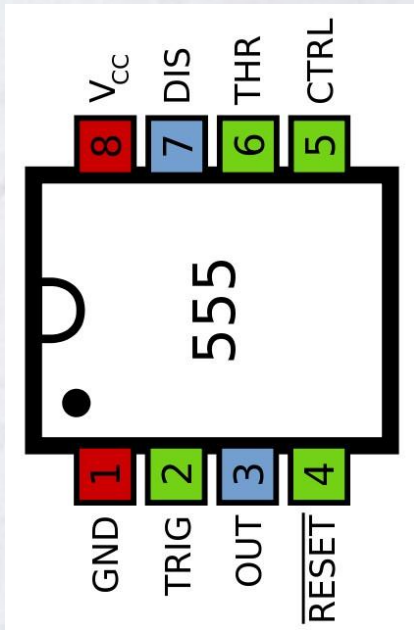

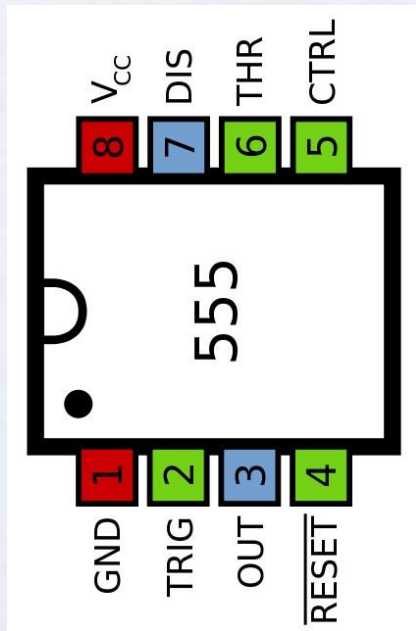



step3


use jumper wire connector pin2 and pin6

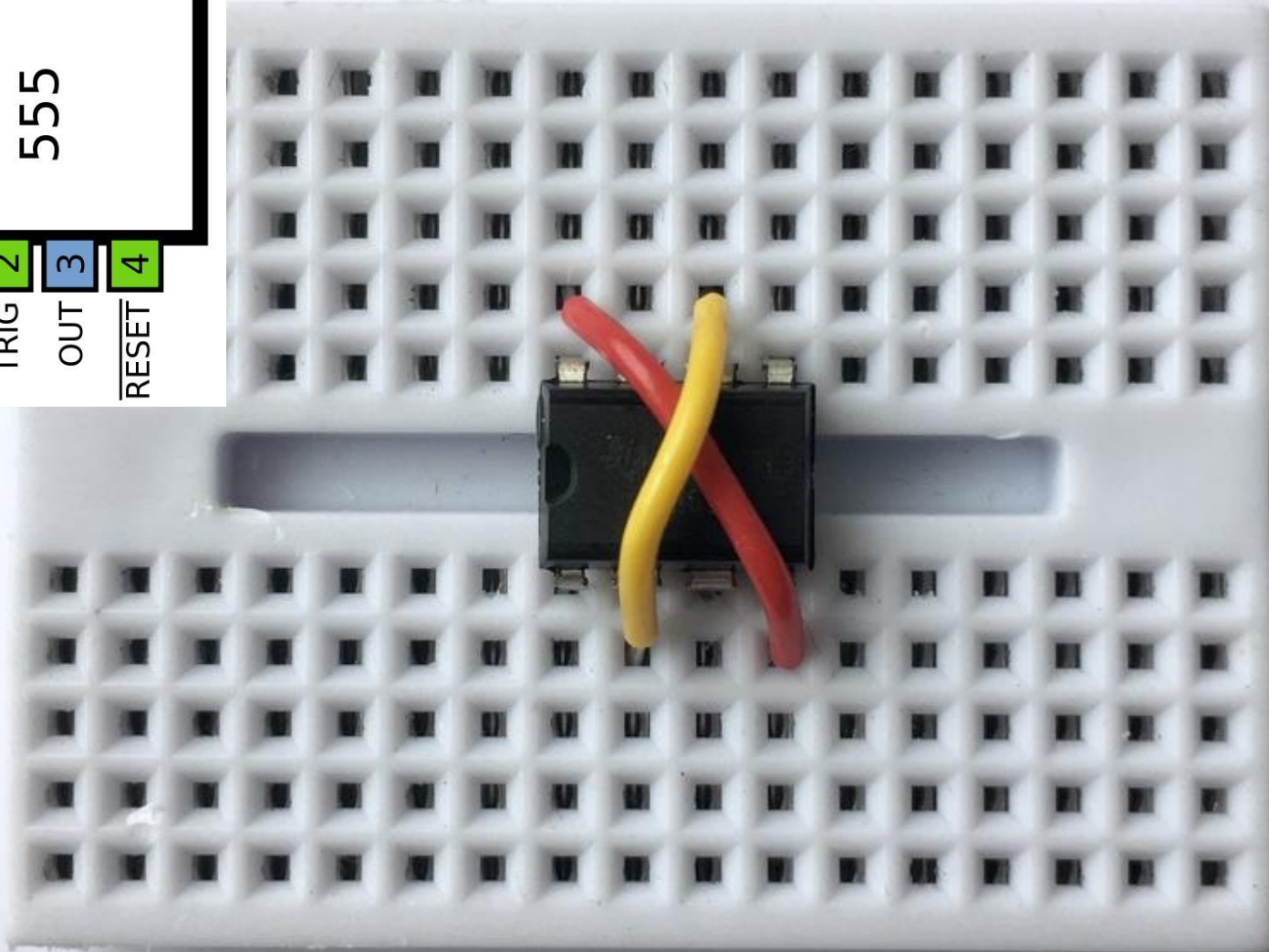

step4

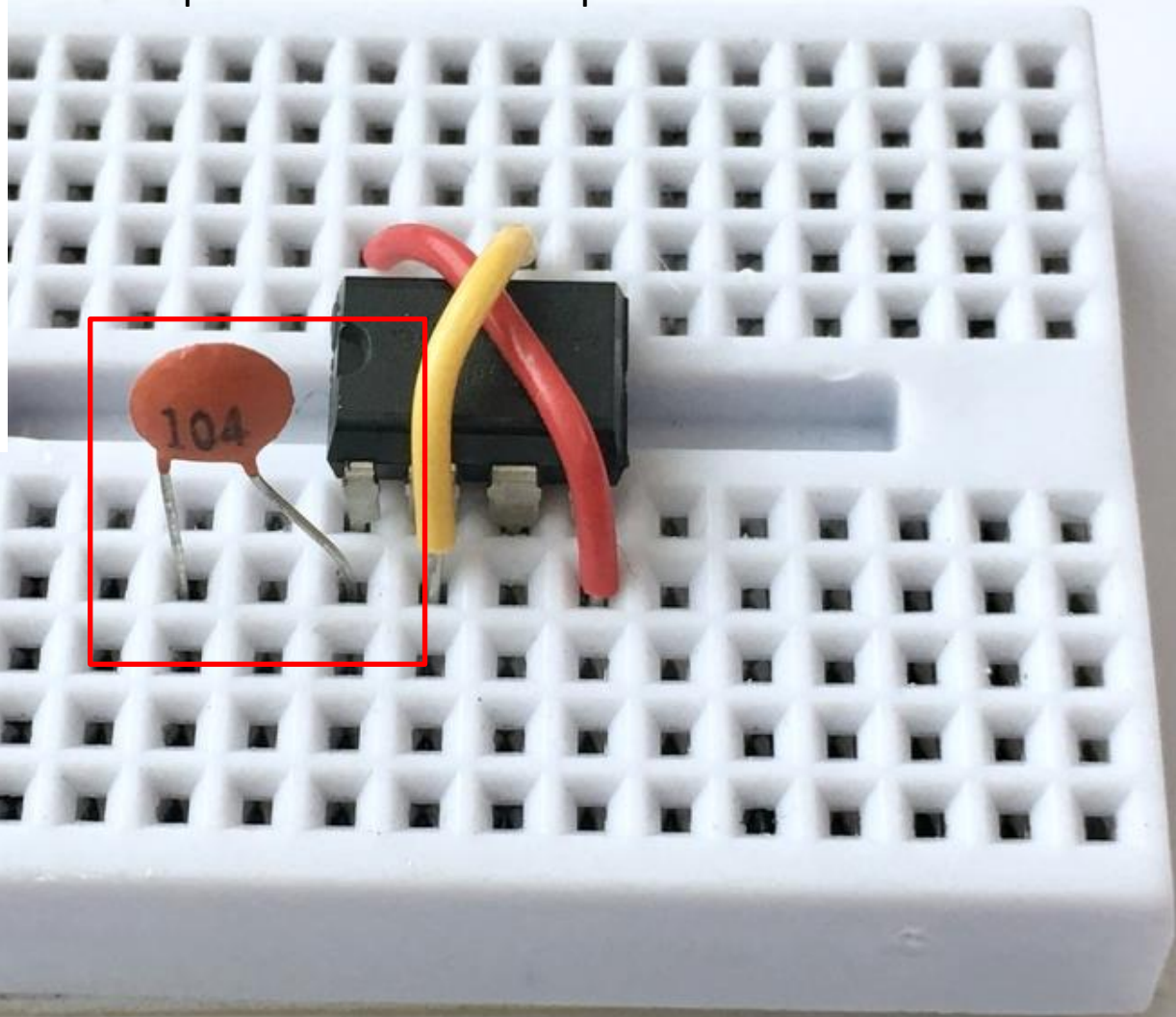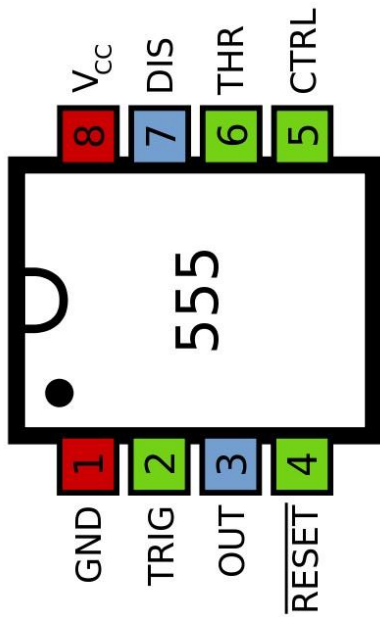
put 0.1uF capacitor on the breadboard. One of the pins connects to 555 pin1



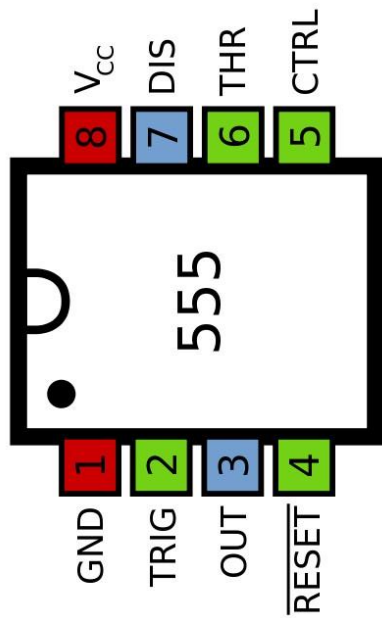

step5

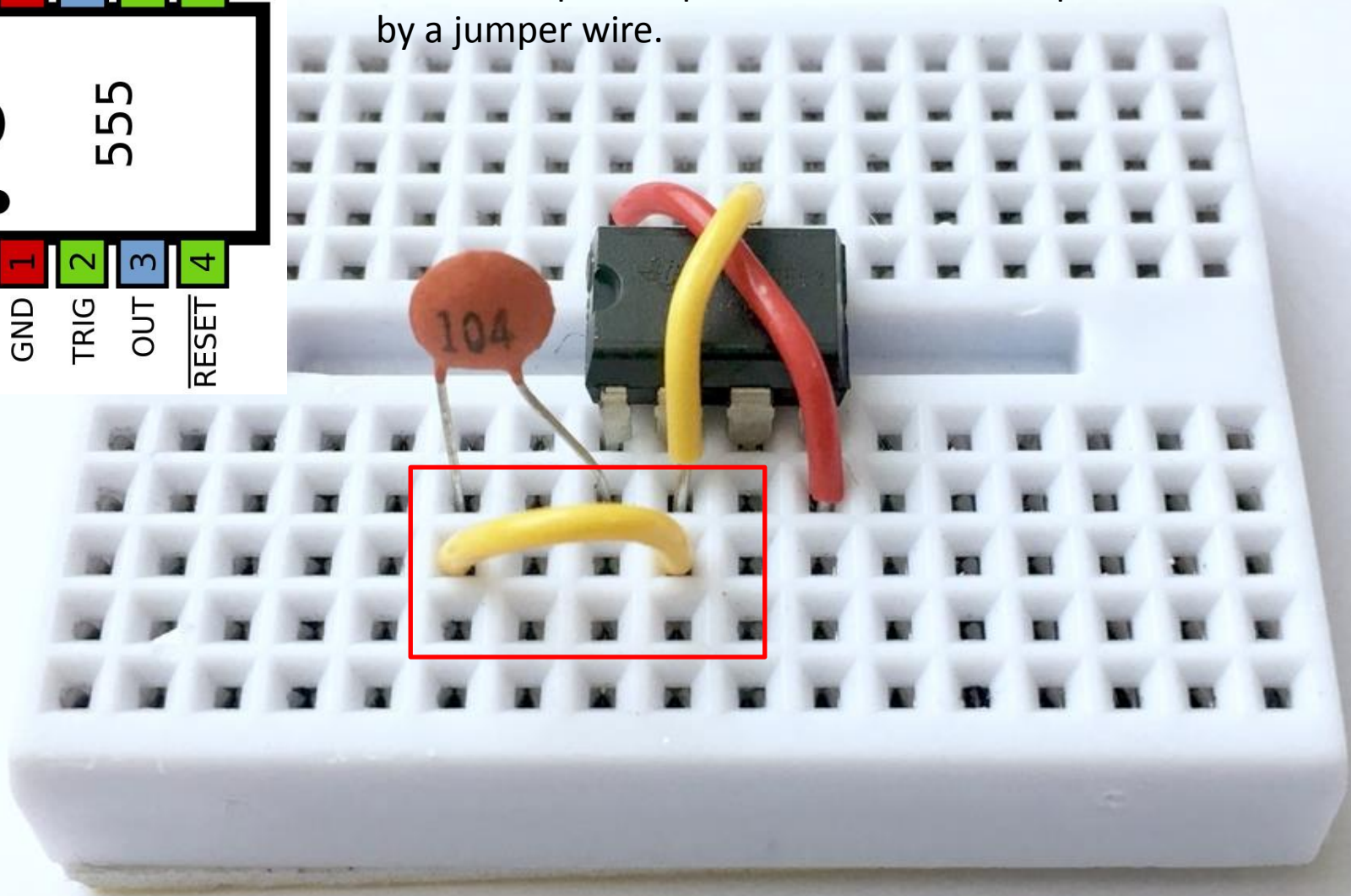
Another capacitor pin connects to 555 IC pin2 by a jumper wire.



step6


put the 20-ohm resistor on the breadboard.

connect the up and down area

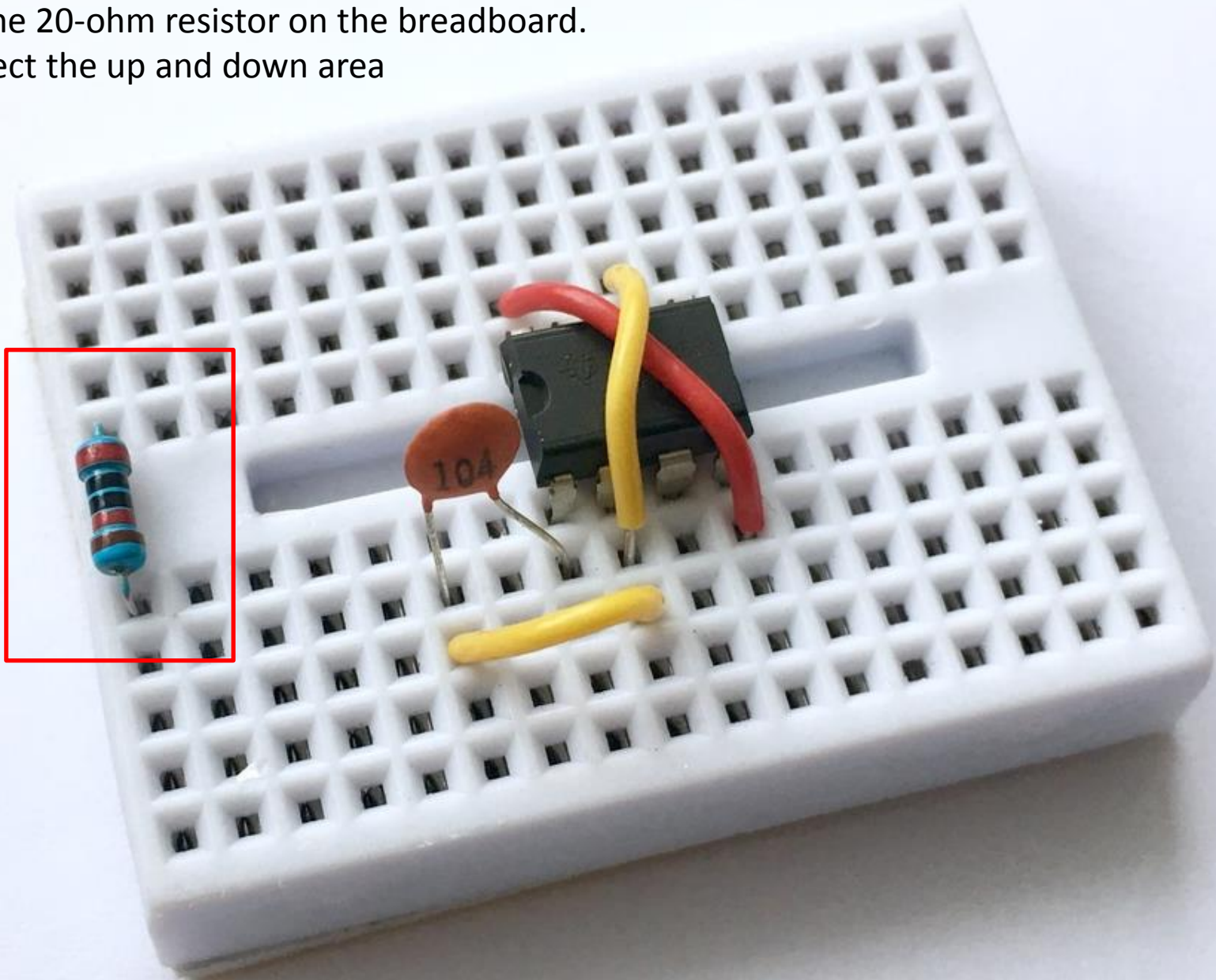

step7

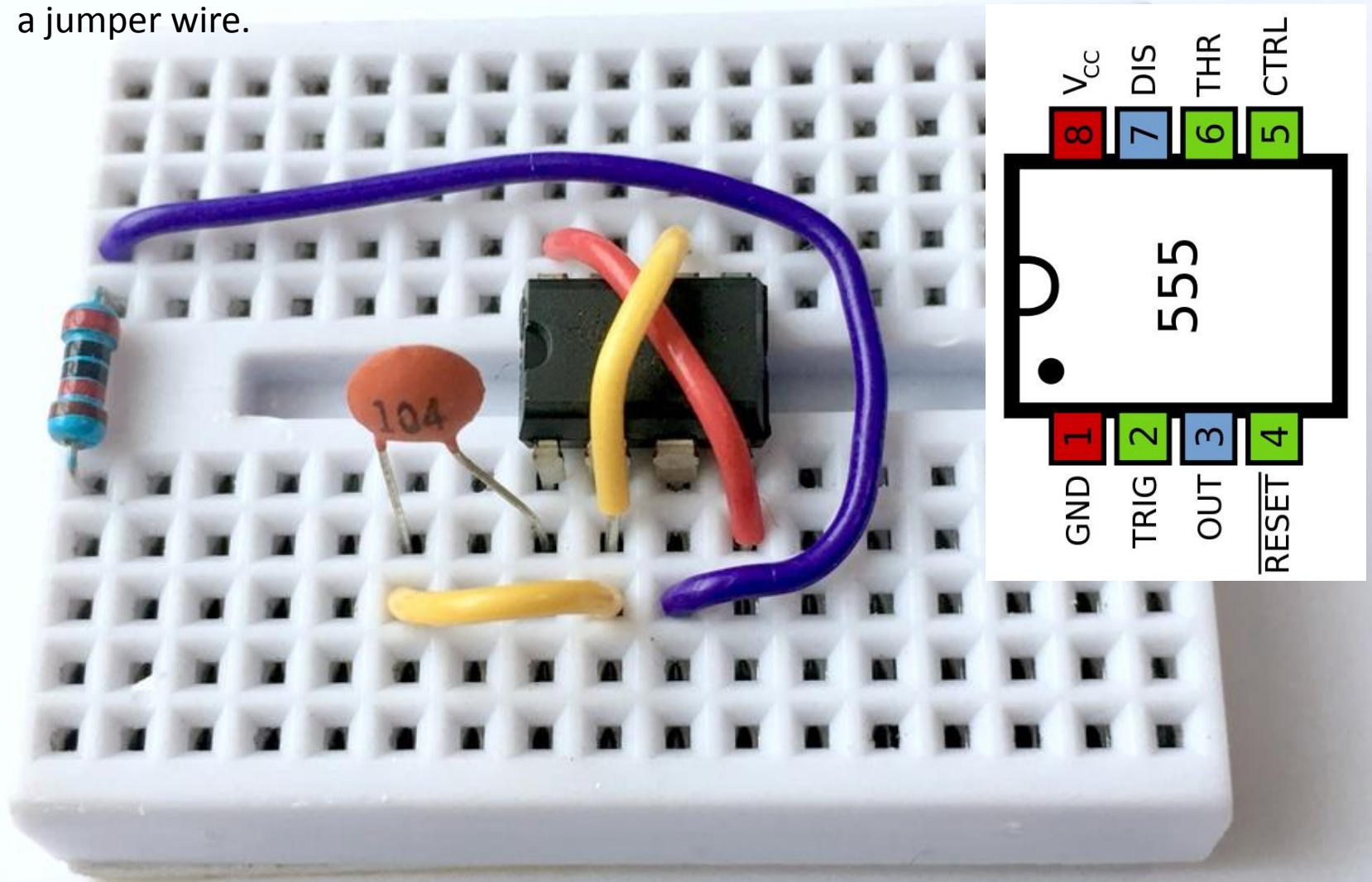connect one of the 20-ohm resistor pin to 555 IC pin3 by a jumper wire.




step8

Connect buzzer:

Black wire to 555 IC pin1.

Red wire to 555 IC pin3.


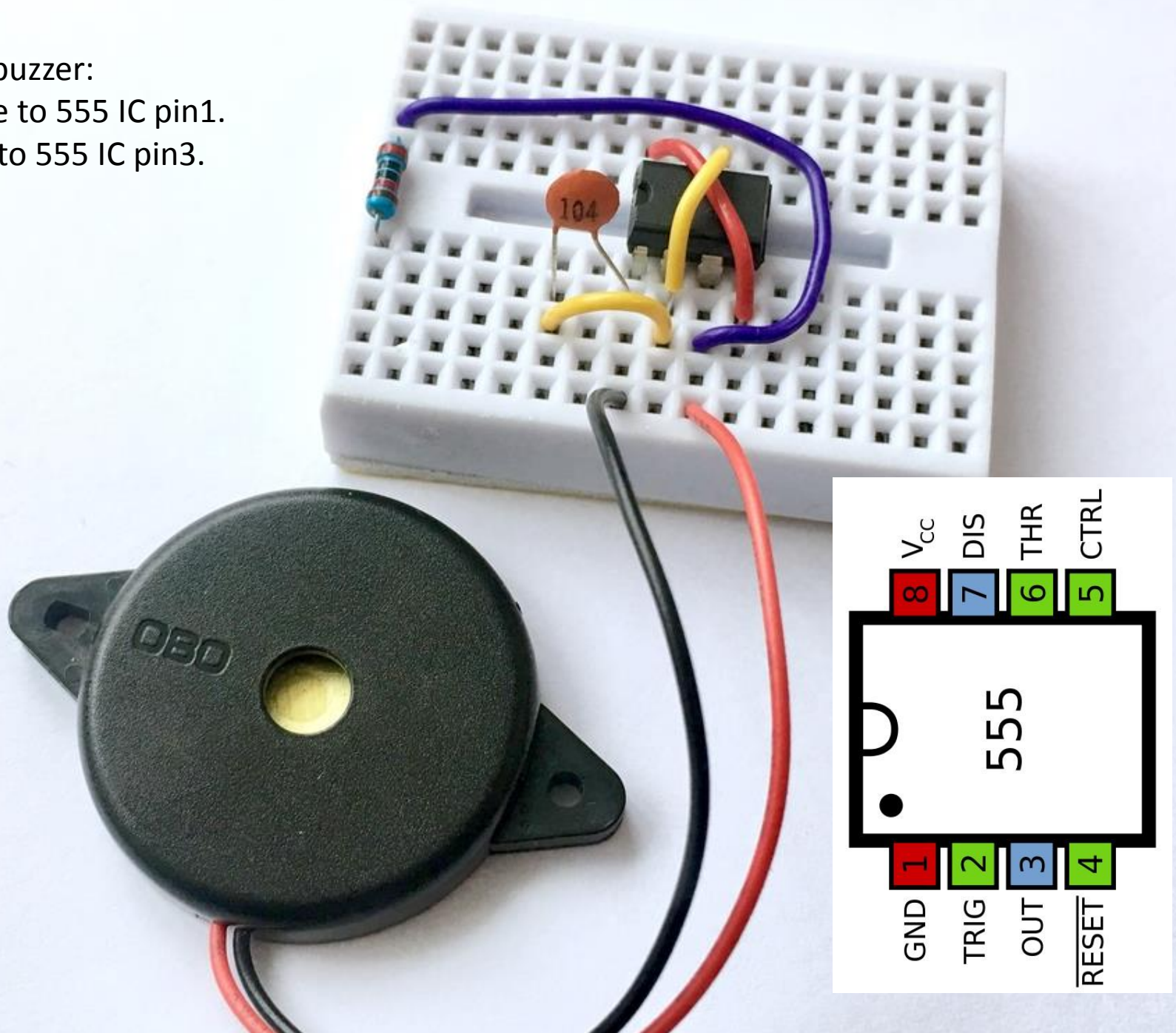


step9

Connect 9V battery:


Black wire to 555 IC pin1.

Red wire to 555 IC pin4.

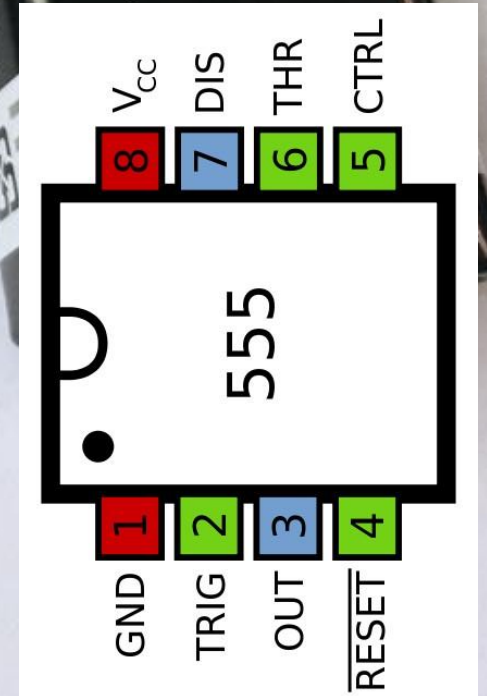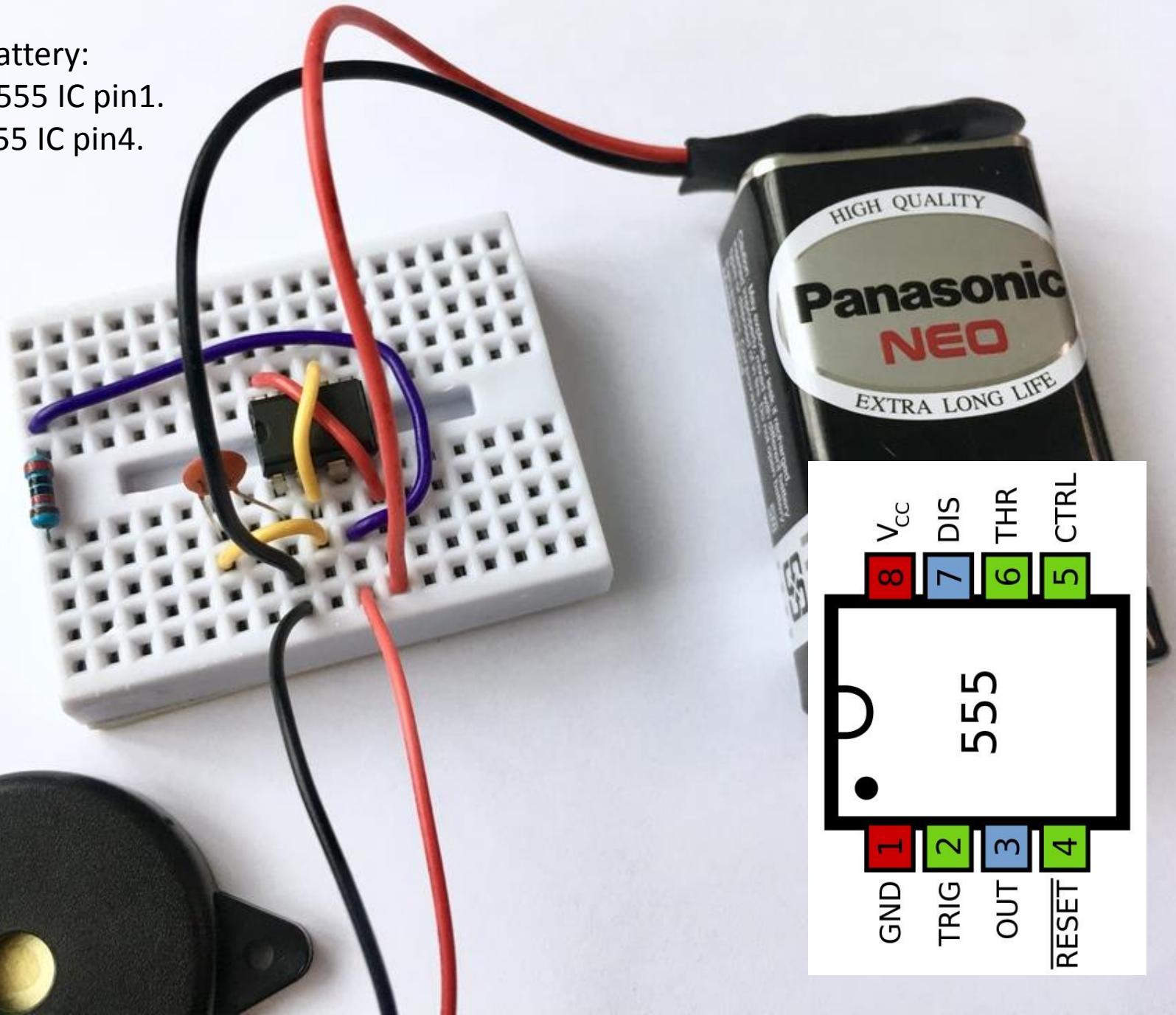


step10

use two long jumper wires as the probes.

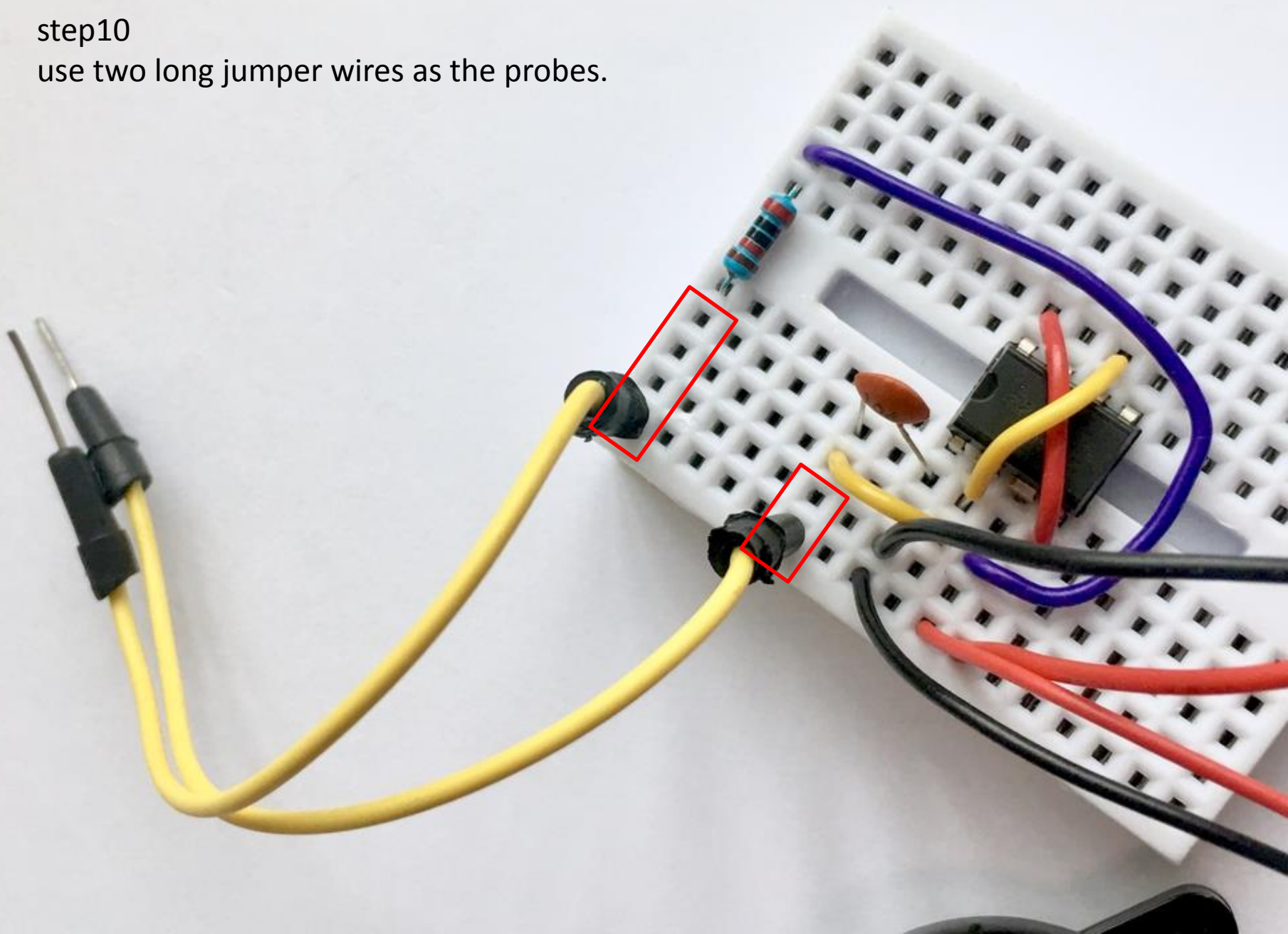


Coqui-Mod 1

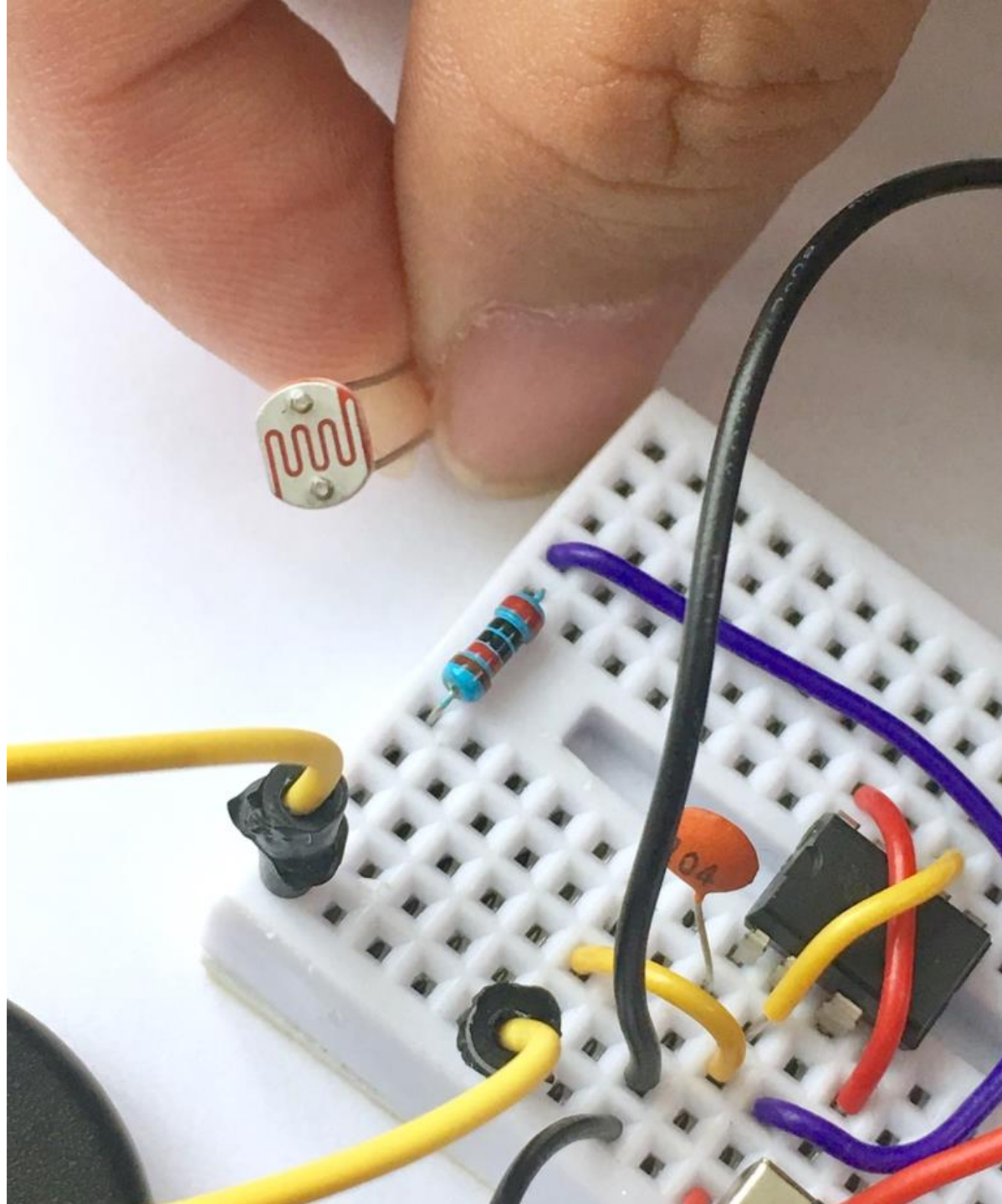

[illegible]

Coqui-Mod 2

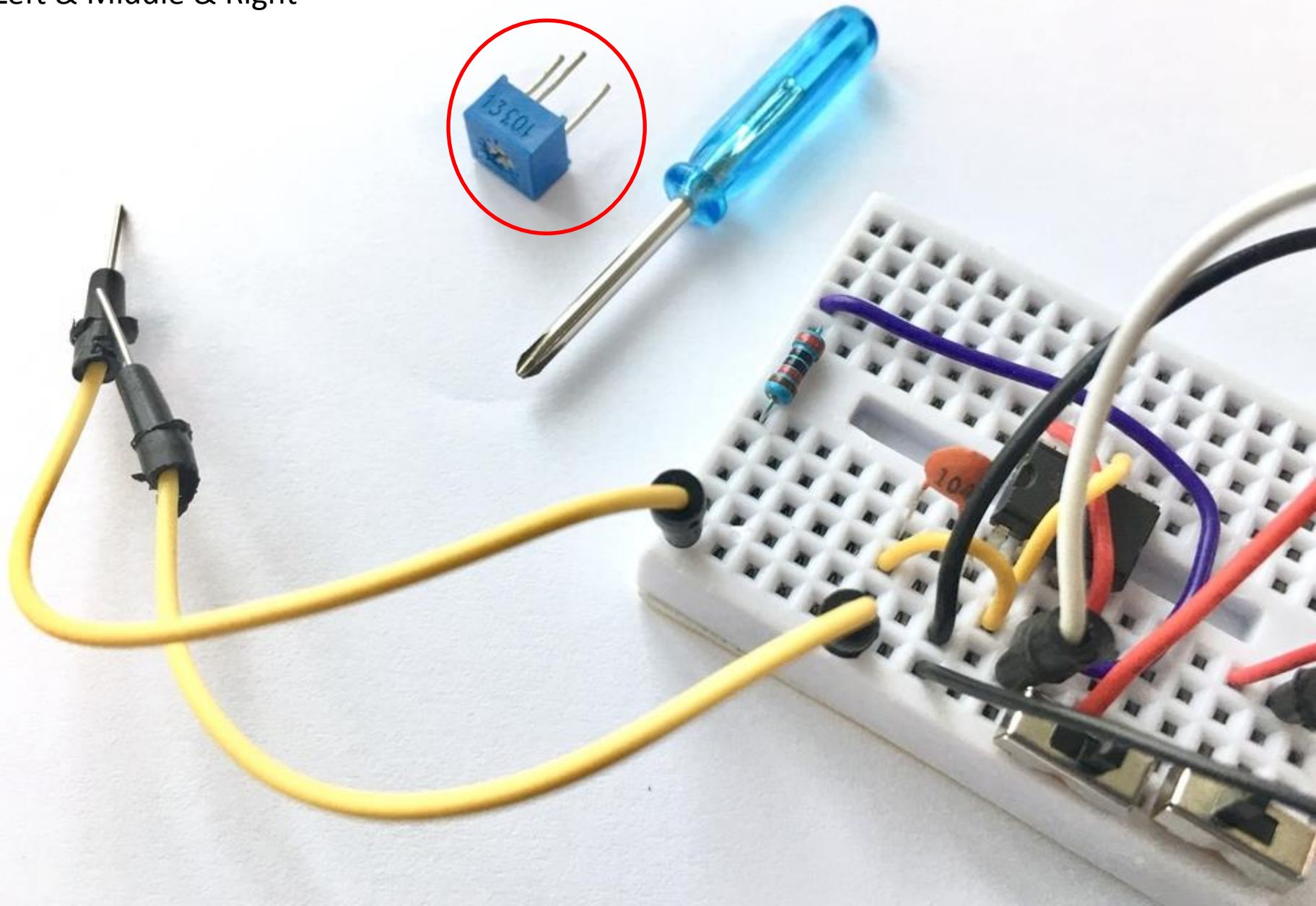
There are 3 pins on potentiometer.
Left & Middle & Right




replace the 20-ohm resistor with a
potentiometer.

I use Left & Middle pins on potentiometer

Remove the 20-ohm resistor

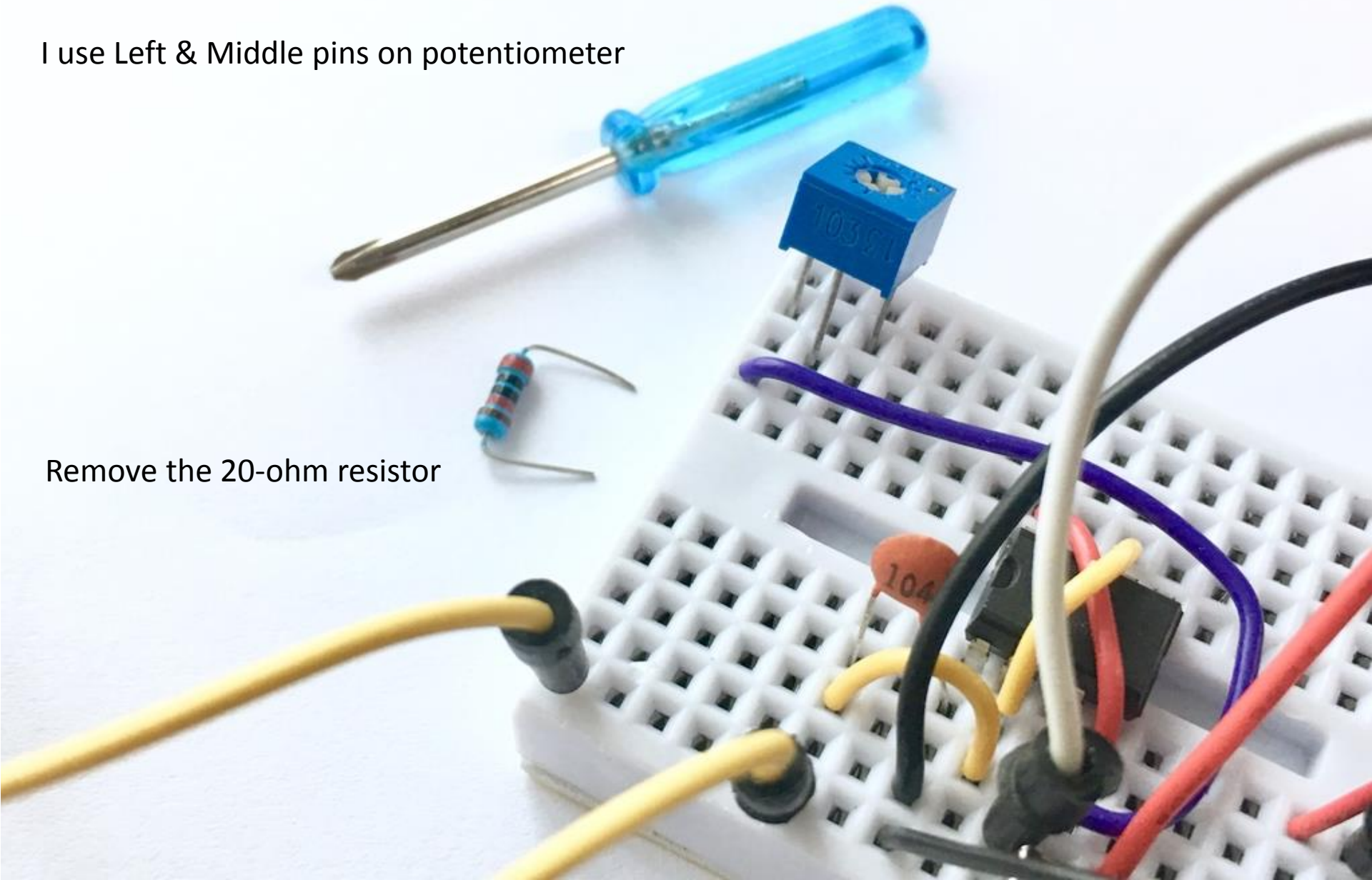

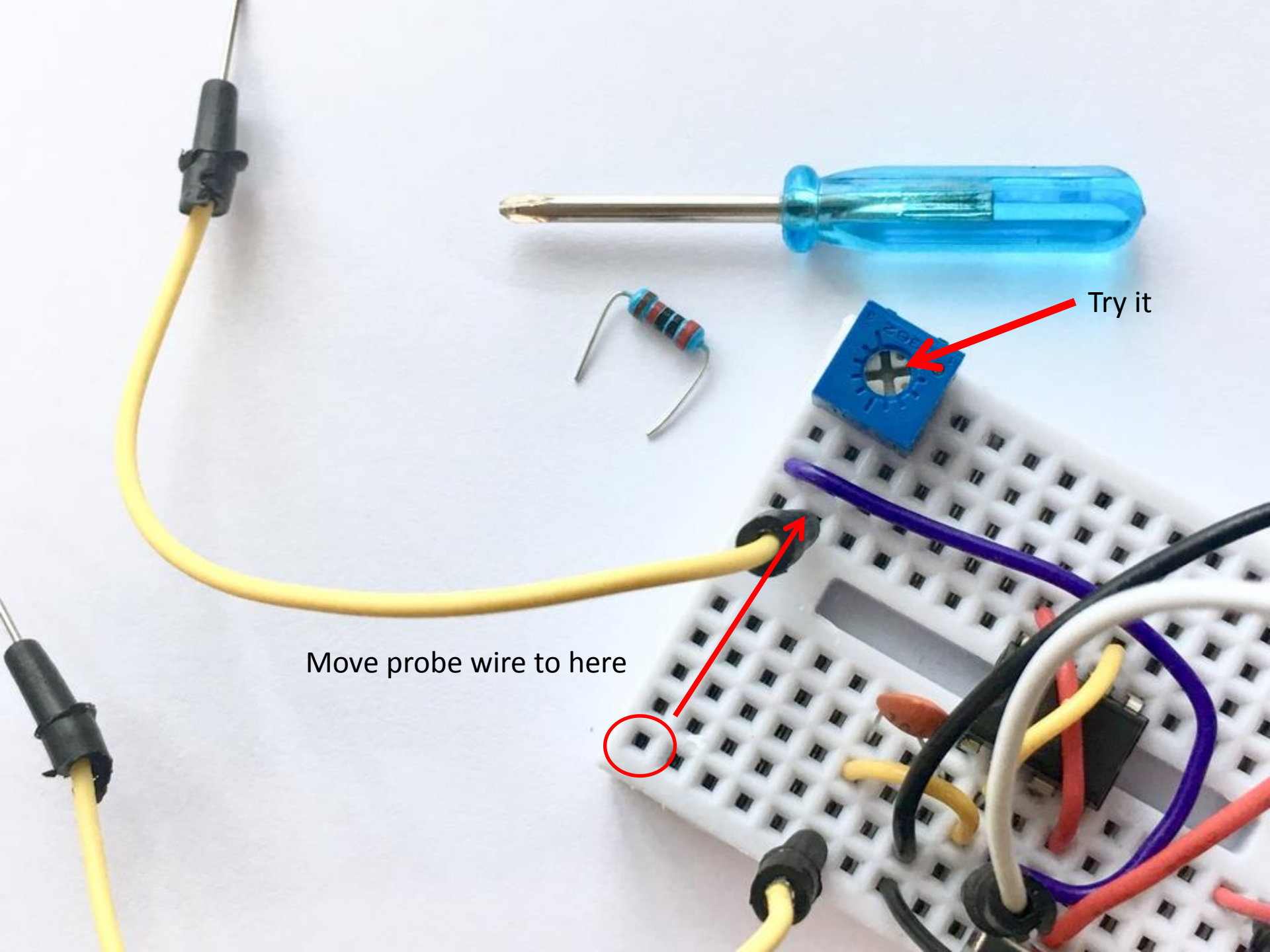


Try it


Move probe wire to here

Coqui-Mod 3




You need a 3.5mm audio output jack.

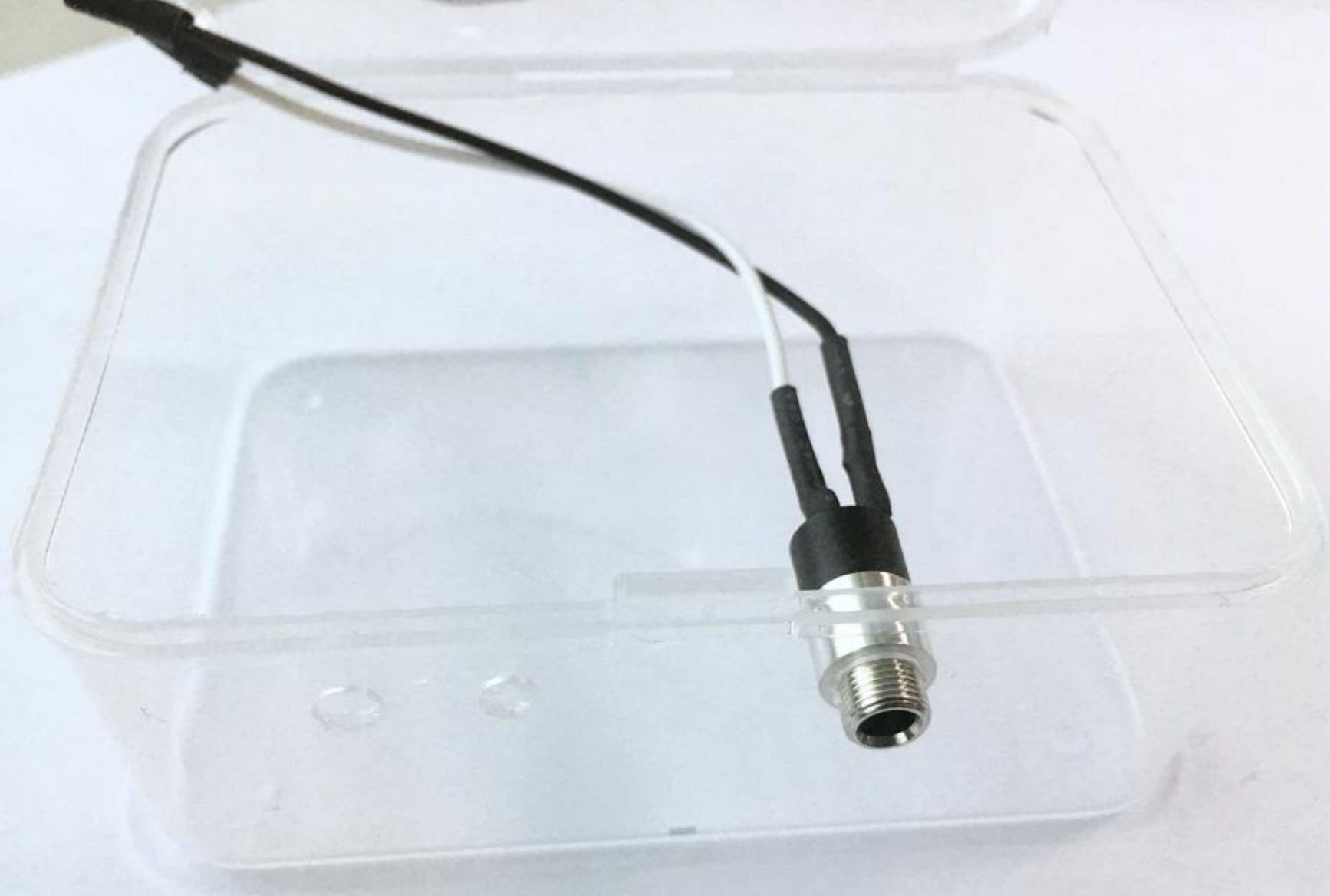

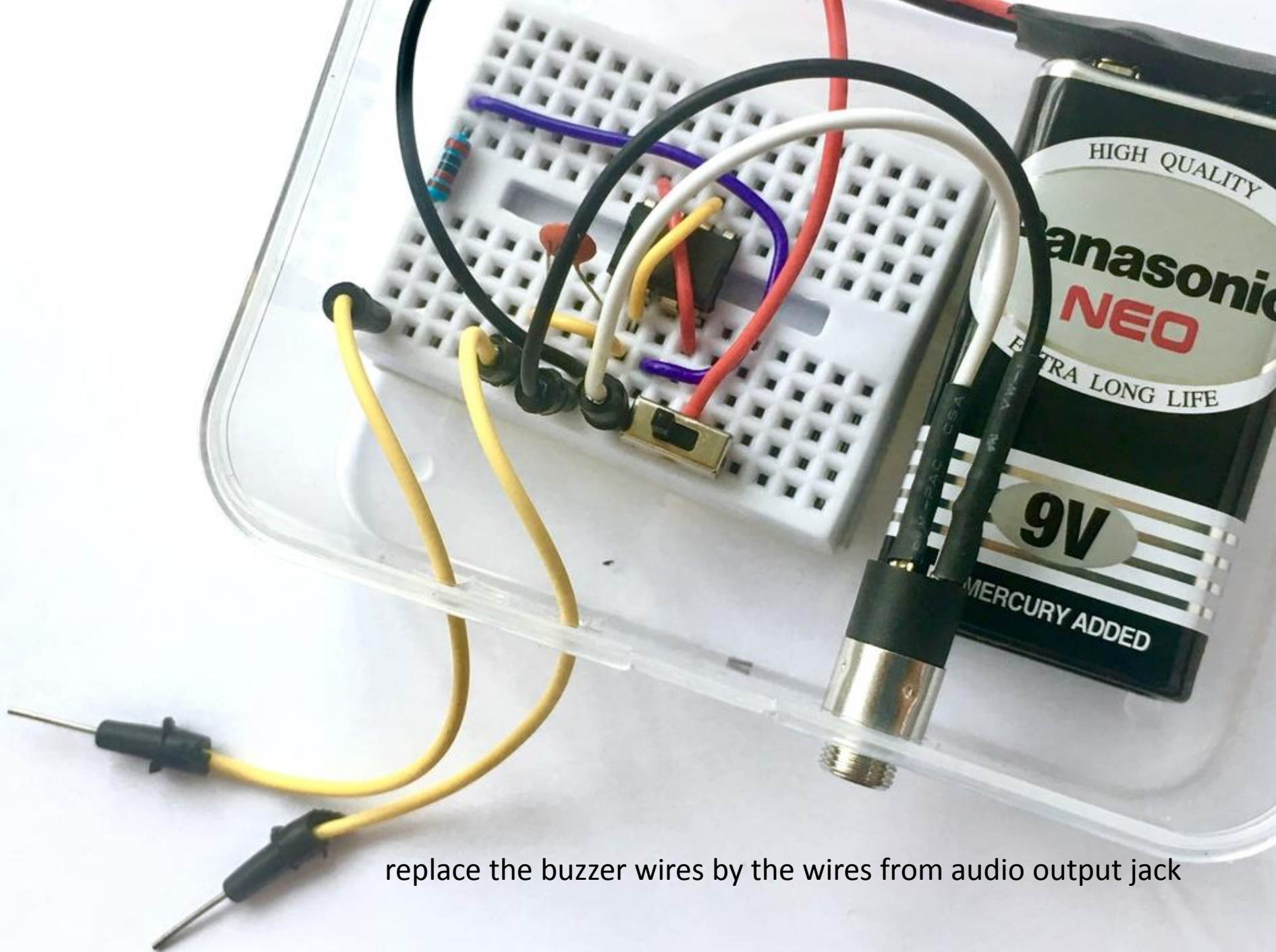

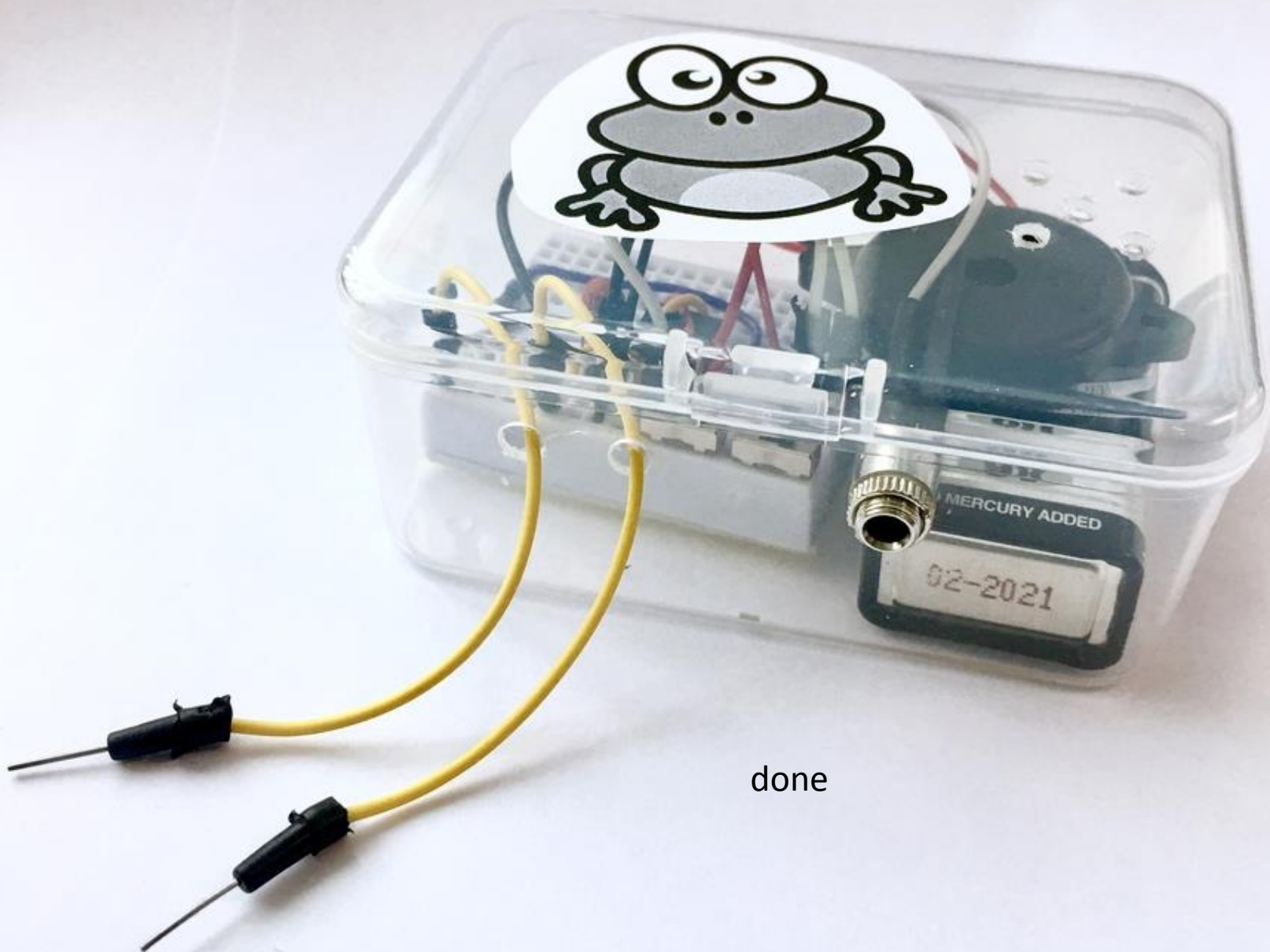replace the buzzer wires by the wires from audio output jack



done

Try it

